

INTERNATIONAL INSTITUTE OF
INFORMATION TECHNOLOGY

H Y D E R A B A D

Lab Report-1

Name: Satkar Juneja

Group No: 37

Teams Group No: 10

Course: Digital Systems and Microcontrollers Lab

Contents

1	Experiment-1	2
1.1	Objective:	2
1.2	Components Required:	2
1.3	Truth Table	3
1.4	Procedure:	4
1.5	Observation:	4
1.6	Conclusion:	4
2	Experiment-2	6
2.1	Objective:	6
2.2	Components Required:	6
2.3	Procedure:	6
2.4	Output:	7
2.5	Conclusion:	8
2.6	TINKERCAD	8
3	Experiment-3	9
3.1	Objective:	9
3.2	Equipment Required:	9
3.3	Procedure:	9
3.4	Output:	10
3.5	Result:	10
3.6	TinkerCAD:	11

1 Experiment-1

1.1 Objective:

- 1) To get familiarized with the digital tool kit
- 2) Using the test kit to implement a not gate

1.2 Components Required:

Breadboard, Power Supply, Not Gate, LED bulbs for input and Output, Switches, Connecting Wires

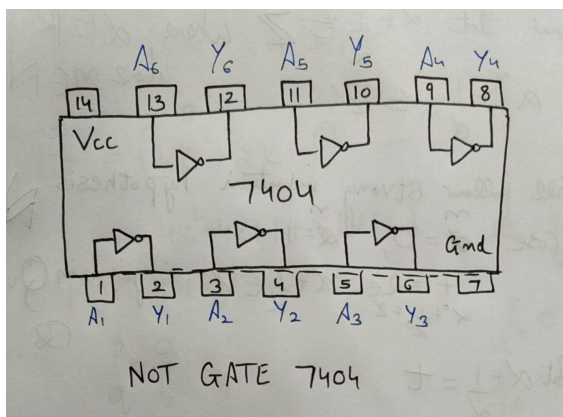


Figure 1: fig 1.2 NOT GATE IC 7404

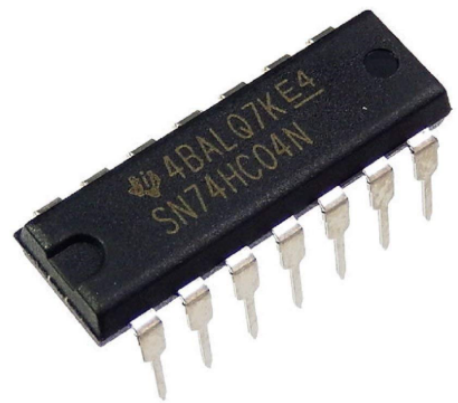


Figure 2: fig 1.3 Another view of IC 7404

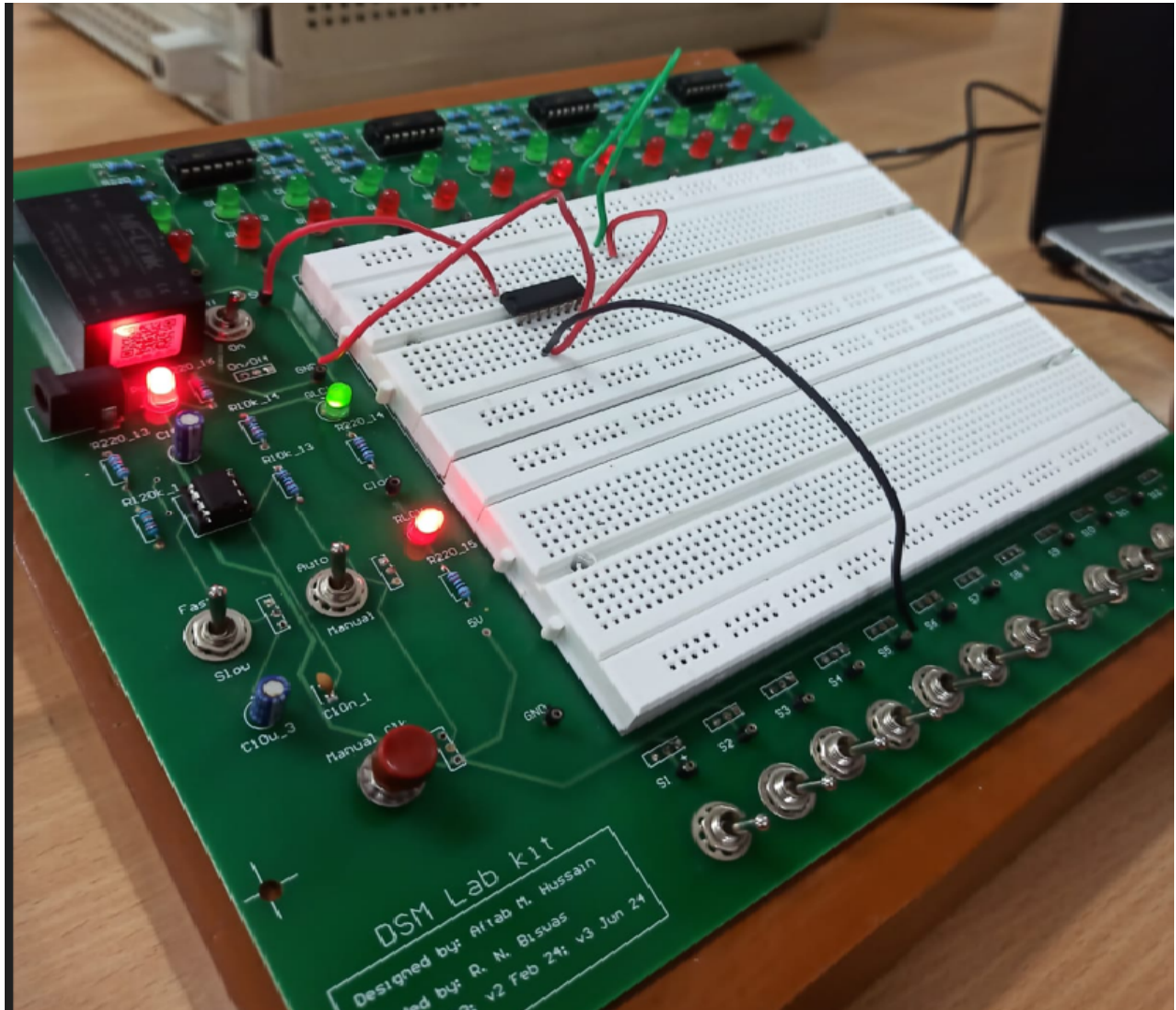


Figure 3: Enter Caption

1.3 Truth Table

Truth table for NOT gate

Input	Output	LED State
0	1	ON (Red)
1	0	OFF (Green)

Table 1: Truth table for NOT gate

Figure 4: Enter Caption

1.4 Procedure:

- 1) On the breadboard, place the IC ,one of the input gates i.e 1,3... will be connected with the input wire.
- 2)Gate Number 14(Labelled Vcc) will be connected to the 5V source.
- 3)Gate Number 7(Gnd) will be connected to the grounding wire.
- 4)The clock control switch will be switched to fast.
- 5)The Vcc supply will be turned on.

1.5 Observation:

As we are using a not gate the output is reversed.

When the switch is turned off we get a red light indicating 1

When it is on we get the green light indicating the output to be a 0

This is exactly the opposite as expected.

1.6 Conclusion:

- 1) NOT gate are simple invertors i.e they convert HIGH voltage to LOW voltage and vice versa

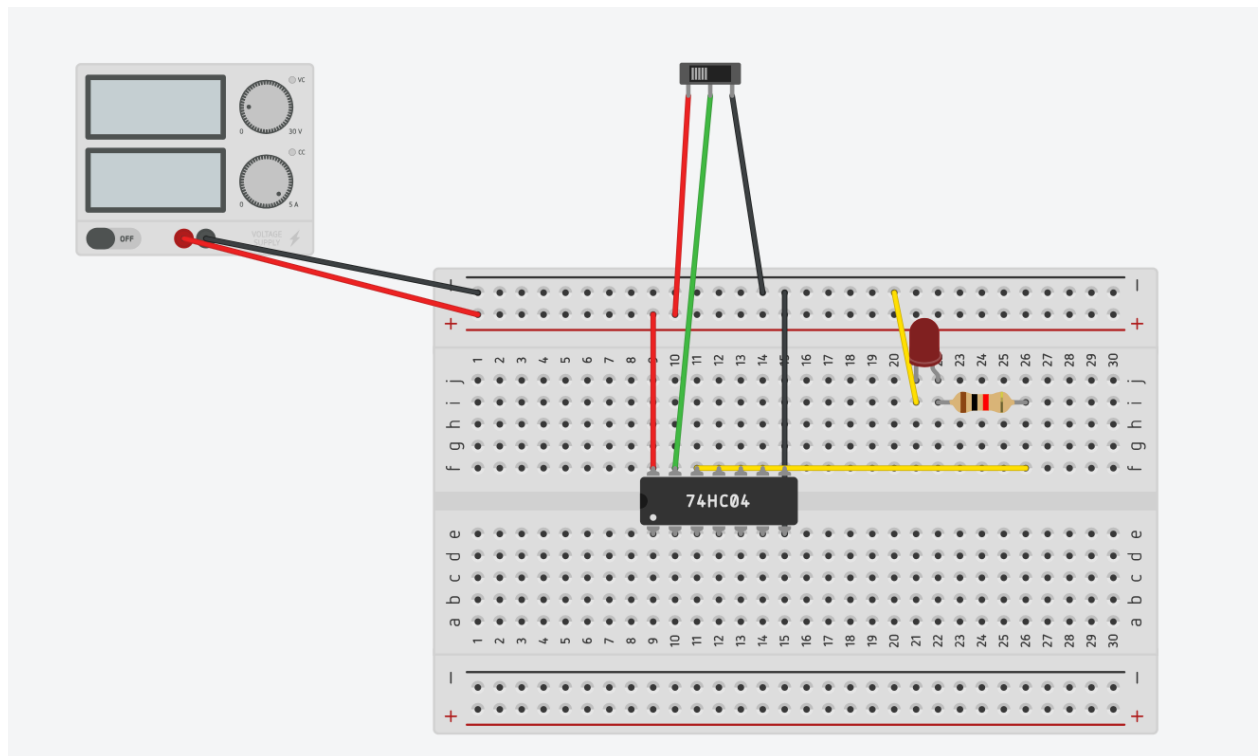


Figure 5: Enter Caption

Link to TinkerCAD:
[Lab1 EX1](#)

2 Experiment-2

2.1 Objective:

- 1) Operate a microcontroller using Arduino IDE
- 2) Use Arduino UNO to print "HELLO WORLD" on the serial monitor if the output of the NOTGATE is 1 and nothing if the output is 0

2.2 Components Required:

Arduino IDE, Arduino UNO, Cable (to connect to a laptop), Hex inverter, Battery

2.3 Procedure:

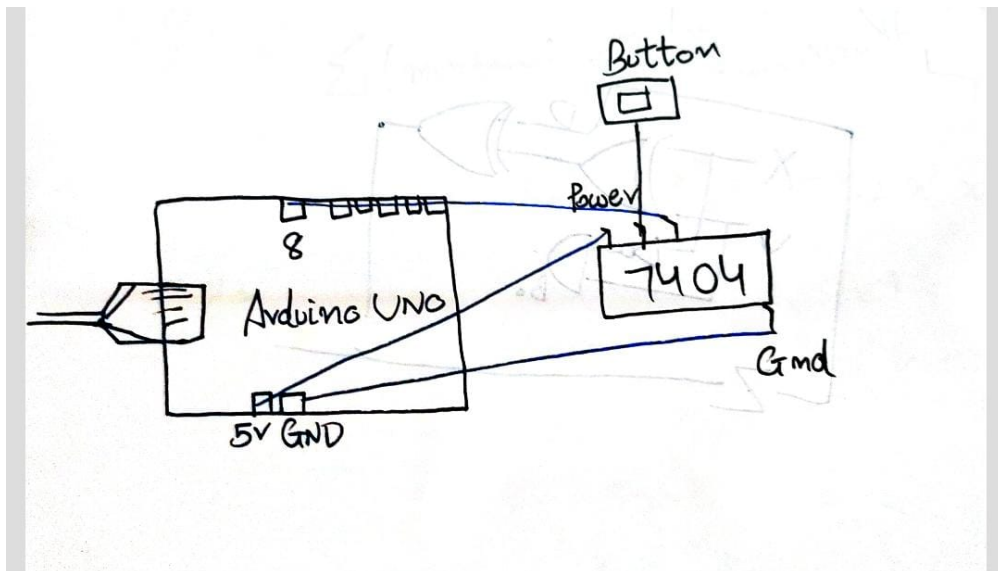


Figure 6:

- 1) Connect the microcontroller to a laptop
- 2) In Arduino IDE configure the connection
- 3) Connect the Hex inverter to the arduino
- 3) Write the code below

```
1  void setup() {  
2      Serial.begin(9600);  
3      pinMode(8, INPUT);  
4  }  
5  
6  void loop() {  
7      int notOutput = digitalRead(8);  
8  
9      if (notOutput == HIGH) {  
10         Serial.println("HELLO WORLD");  
11     } else {  
12         Serial.println("");  
13     }  
14  
15     delay(1000);  
16 }  
17
```

Figure 7: Hello World

2.4 Output:



Figure 8: Output

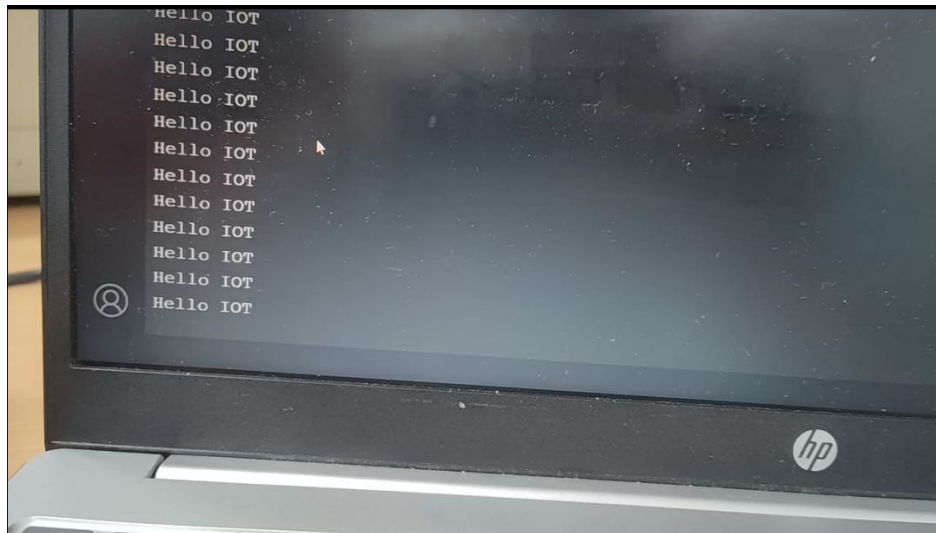


Figure 9: We printed Hello IOT for example

2.5 Conclusion:

microcontrollers are simple to operate but can perform a great variety of tasks

2.6 TINKERCAD

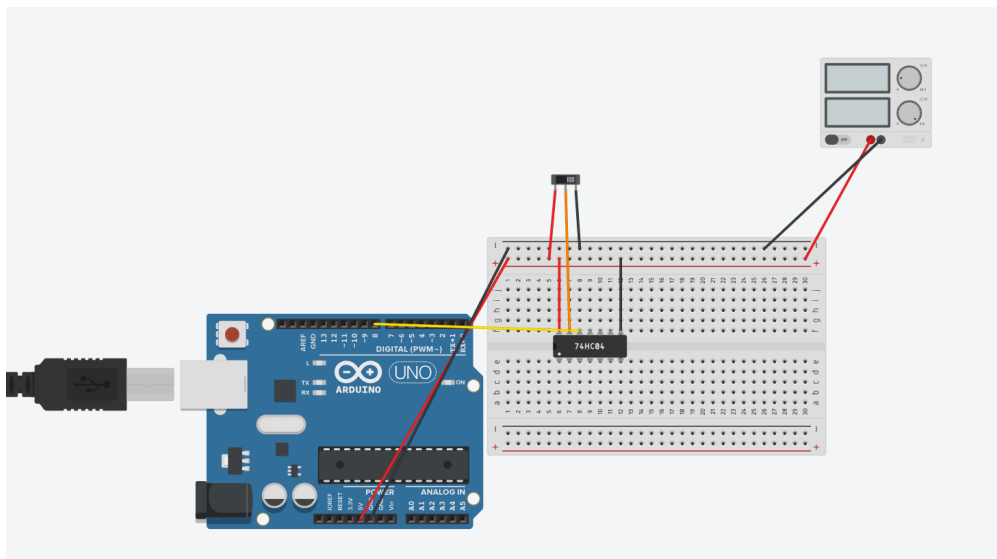


Figure 10: Tinkercad

[Link](#)

3 Experiment-3

3.1 Objective:

Use Arudino UNO to control and operate an LED

3.2 Equipment Required:

Arduino UNO,Arduino IDE,connecting wires,LED,Breadboard

3.3 Procedure:

- 1)Launch Arduino IDE
- 2)Set the LED on the breadboard
- 3)Connect the smaller end to GND on the board
- 4) the longer end to an output of your choice for example 8
- 5) write the following code on the IDE
- 6)Push the code to the board

```
Unsaved - sketch_aug15c.ino  LED_PIN 8
2  void setup() {
3      // put your setup code here, to run once:
4      pinMode(8,OUTPUT);
5
6  }
7
8  void loop() {
9      // put your main code here, to run repeatedly:
10     digitalWrite(8, HIGH);
11     delay(1000);
12     digitalWrite(8, LOW);
13     delay(1000);
14
15 }
16
```

Figure 11: Instructions

3.4 Output:

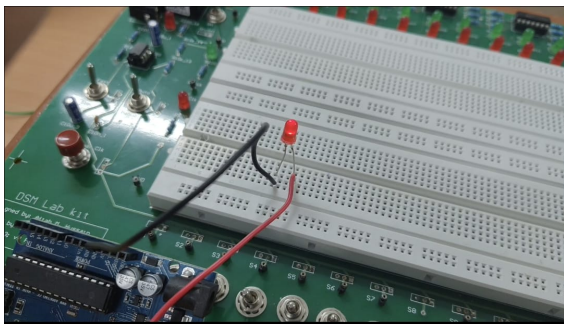


Figure 12: ON

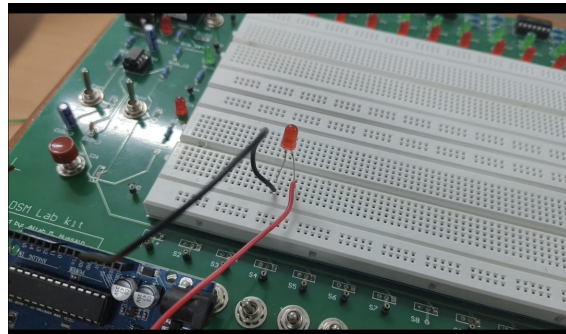


Figure 13: OFF

3.5 Result:

From the code the following can be observed:

- 1) Output is taken from the 8th outlet

2) There is a 1 second or a 1000ms delay in the blinking of the LED

3.6 TinkerCAD:

<https://www.tinkercad.com/things/7pD8WVQIa46-experiment-3>