

International Institute of Information Technology, Hyderabad

EC2.101 - Digital Systems and Microcontrollers

Model Exam - Grading Rubric & Solutions Outline (Unofficial)

General Instructions to Graders

- **Process over Product:** For design questions, full marks should be awarded for correct logic and minimization steps (K-Maps), even if a minor transcription error occurs in the final circuit drawing.
- **Transistor Counts:** Allow for small variations in transistor counts if the student uses a valid alternative topology (e.g., Transmission gates vs. standard CMOS), provided they state their assumptions.
- **Assembly Code:** Logic and comments are more important than exact syntax, provided the pseudo-code/mnemonics align with the instruction set provided in the course.

Detailed Marking Scheme

Q. No	Expected Solution & Criteria	Marks
Q1. Base System Concepts [15 Marks]		
1(a)	Base-5 Even/Odd Proof <ul style="list-style-type: none">• Student represents number as $N = 5k + r$.• Mathematical Argument: Since 5 is odd, $5k$ alternates parity depending on k. Therefore, r (LSD) alone is insufficient to determine total parity.• Counter-example provided (e.g., $(12)_5 = 1 \times 5 + 2 = 7$ which is Odd, but LSD is 2 which is Even).	[5] [1] [2] [2]
1(b)	Base-3 Divisibility Logic <ul style="list-style-type: none">• Truth Table construction: Inputs 4 bits (representing two ternary digits A_1A_0), Output 1 if Value % 4 == 0. <i>Note: Input combinations representing digits ≥ 2 must be treated as Don't Cares (X).</i>• K-Map Simplification: Correct grouping including Don't Cares.• Final Circuit Drawing: Logic gates matching the expression.	[10] [3] [4] [3]
Q2. Arithmetic Optimization [15 Marks]		
2(a)	Absolute Difference $A - B$ <ul style="list-style-type: none">• Truth Table: 4 inputs (A=2 bits, B=2 bits), 2 outputs.• K-Maps: Separate maps for Output Bit 0 and Bit 1.• Minimized Expressions: Correct SOP or POS equations.	[8] [2] [3] [3]
2(b)	CMOS Implementation & Comparison <ul style="list-style-type: none">• CMOS Schematic: Correct Pull-up (PMOS) and Pull-down (NMOS) networks corresponding to the logic.• Transistor Count (Custom): Calculation based on the schematic.• Comparison: Correctly estimating transistors for (Adder + XORs for inversion) and concluding which is smaller.	[7] [3] [2] [2]
Q3. Sequential Design (Fibonacci) [15 Marks]		
3(a)	JK Counter Design <ul style="list-style-type: none">• State Sequence: Identifying states ($0000 \rightarrow 0001 \rightarrow 0010 \rightarrow 0011 \rightarrow 0101 \rightarrow 1000 \rightarrow 1101 \rightarrow 0000$).• Excitation Table: Correct use of JK excitation ($0 \rightarrow 0, 0 \rightarrow 1, 1 \rightarrow 0, 1 \rightarrow 1$).	[10] [2] [2]

	<ul style="list-style-type: none"> • K-Maps: 4 maps (or 8 for separate J and K) solving for inputs. • Circuit/Equation: Correct expressions for J_A, K_A, etc. 	[4] [2]
3(b)	Self-Correction <ul style="list-style-type: none"> • Unused States Identification: Listing states not in Fibonacci sequence (e.g., 4, 6, 7, 9...). • Logic Implementation: Ensuring 'Next State' for these unused states points to '0000' or a valid sequence state. 	[5] [2] [3]
Q4. Circuit Analysis [10 Marks]		
4(a)	Timing Diagram <ul style="list-style-type: none"> • Correct initialization (0000). • Correct shifting behavior for first 3 cycles. • Correct handling of the inverted feedback ($E' \rightarrow A$). • Correct handling of the clock gating (B' driving C's clock). 	[4] [1] [1] [1] [1]
4(b)	State Diagram <ul style="list-style-type: none"> • Identifying all valid states in the loop. • Identifying the cycle length (how many states before repeat). 	[4] [3] [1]
4(c)	Johnson Counter Theory <ul style="list-style-type: none"> • Correct formula stated ($2k$ or $2n$ states). 	[2] [2]
Q5. Microcontroller Assembly [10 Marks]		
5(a)	Search Algorithm Code <ul style="list-style-type: none"> • Initialization: Loading pointers (0x200, 0x201) and Loop Counter (from 0x220). • Fetch Loop: Correctly incrementing memory pointer and fetching data. • Comparison Logic: Subtraction or XOR to check equality with Target V. • Control Flow: Branch if Zero (Match found) vs Branch if Counter $\neq 0$ (Continue). 	[10] [2] [3] [3] [2]
Q6. Conversions [5 Marks]		
6	Calculations <p>(a) $(45.6)_{10} \rightarrow$ Binary (101101.1001...).</p> <p>(b) Base 5 \rightarrow Base 8 (Intermediate Base 10 step implied: $123_5 = 38_{10} = 46_8$).</p> <p>(c) 2's Complement Subtraction ($1001 + (0101)$... check for overflow).</p> <p>(d) Signed Mag (10001111) and 2's Comp (11110001).</p>	[5] [1] [1] [1] [2]