



**INTERNATIONAL INSTITUTE OF
INFORMATION TECHNOLOGY**

H Y D E R A B A D

Lab Report-6

Name: Satkar Juneja

Group No: 37

Teams Group No: 10

Course: Digital Systems and Microcontrollers Lab

Contents

1 RS Latch	1
1.1 Objective	1
1.2 Equipment Required	1
1.3 Procedure	1
1.3.1 Setup	1
1.3.2 Testing	1
1.4 Schematic	2
1.5 LAB Photo	2
1.6 TinkerCAD	3
1.7 Conclusion	3
2 Master Slave Flip-Flop	4
2.1 Objecctive	4
2.2 Equipment Required	4
2.3 Procedure	4
2.3.1 Master	4
2.3.2 Slave	4
2.3.3 Testing	5
2.4 Schematic	5
2.5 LAB Photo	6
2.6 TinkerCAD	6
2.7 Conclusion	6
3 4-Bit Up-Down Counter	6
3.1 Objective	7
3.2 Equipment Required	7
3.3 Procedure	7
3.3.1 Setup	7
3.3.2 Code	7
3.4 Schematic	8
3.5 Lab Photo	9
3.6 TinkerCAD	9
3.7 Conclusion	10

1 RS Latch

1.1 Objective:

To Assemble a latch using NOR gates

1.2 Equipment Required

1. Digital Test Kit
2. NOR Gate(CD4001)
3. Connecting Wires
4. Vcc and GND

1.3 Procedure

1.3.1 Setup

1. Place the IC on the breadboard
2. Connect the Vcc and the GND
3. Connect the Inputs to S and R
4. Connect the Other Input of the NOR gate to the Output of the Other gate
5. Show the output Q through an LED

1.3.2 Testing

S	R	Q
0	1	0
0	0	0
1	0	1
0	0	1
0	1	0
1	0	1
0	1	0
0	0	0
1	1	Forbidden Input
0	0	0
1	0	1
1	1	Forbidden Input
0	0	0
0	1	0
1	1	Forbidden Input
0	0	0

Table 1: Testing Sequence

1.4 Schematic

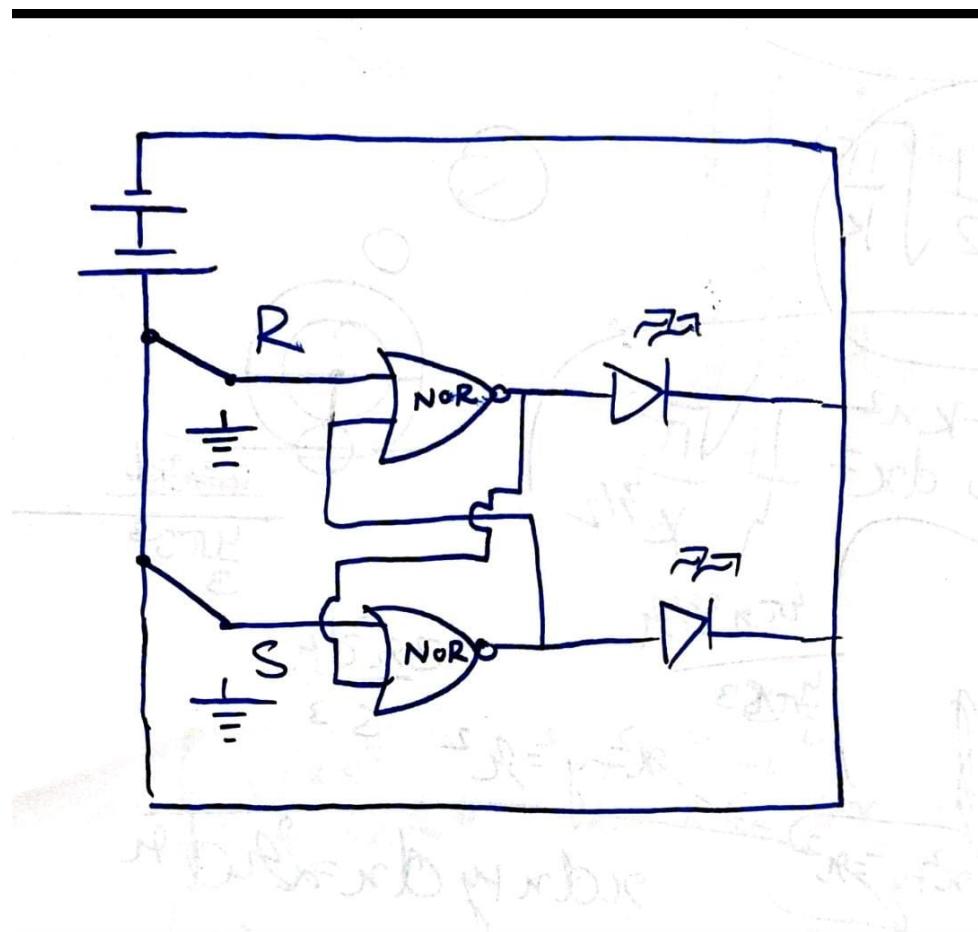


Figure 1: Schematic

1.5 LAB Photo

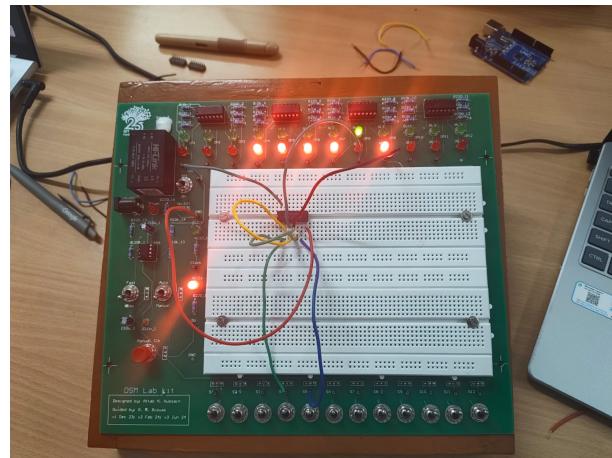


Figure 2: Lab Photo

1.6 TinkerCAD

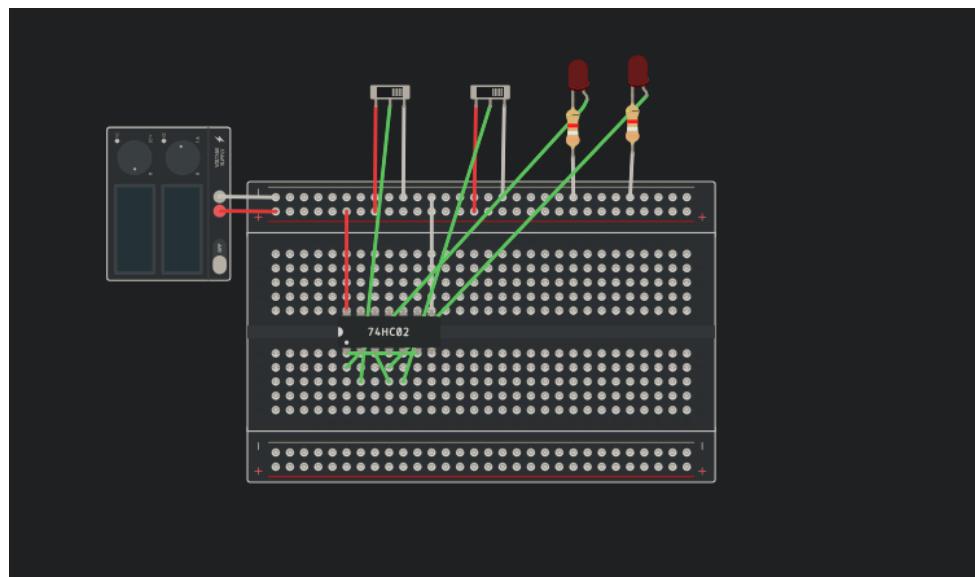


Figure 3: TinkerCAD

Here

1.7 Conclusion

We have successfully Checked the Working of an RS latch.

2 Master Slave Flip-Flop

2.1 Objeective

To Design a Master Slave Flip-Flop using NAND(CD4012) and NOR(CD4001) gates

2.2 Equipment Required

1. Digital Test Kit
2. NAND(CD4012)
3. NOR(CD4001)
4. Connecting Wires
5. Vcc and GND

2.3 Procedure

2.3.1 Master

1. Place the IC's on the Breadboard
2. Connect the Vcc and The GND
3. Connect the Input J and K
4. Connect the Clock to the first set of NAND gates
5. Connect the outputs of these NAND gates to the second set and label them as $S_{M'}$ and $R_{M'}$
6. Connect the Output of one NAND gate to the input of the other
7. label these outputs as Q_M , Q'_M
8. Label the final outputs as Q and Q'

2.3.2 Slave

1. Connect Q_M and Q'_M to the inputs of the NOR gate with the clock as the other input
2. label these inputs as R_S and S_S
3. as in the master connect the outputs to the inputs of the NOR gates

2.3.3 Testing

J	K	Action	$Q(n + 1)$
0	0	HOLD	Q
0	1	CLEAR	0
1	0	SET	1
1	1	TOGGLE	Q'

Table 2: Testing Table

$$R_M = K \cdot Q \cdot Clk \quad S_M = J \cdot Q' \cdot Clk' \quad R_S = Q'_M \cdot Clk'$$

2.4 Schematic

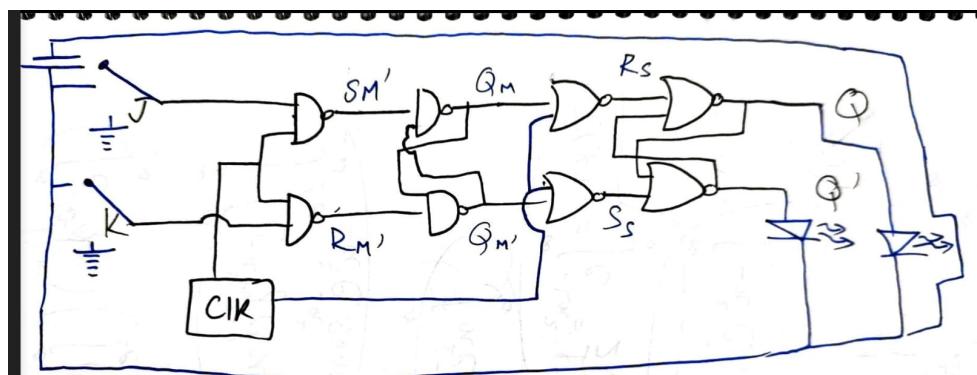


Figure 4: Schematic

2.5 LAB Photo

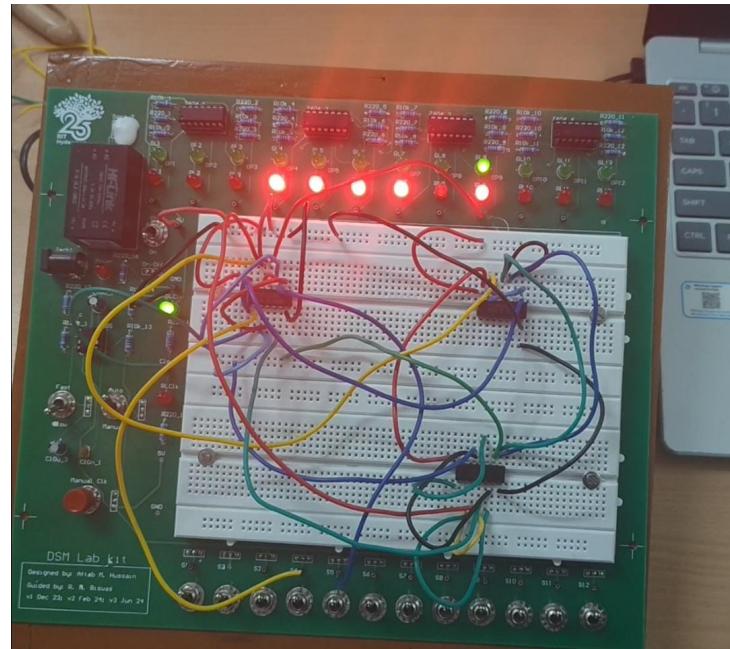


Figure 5: LAB Photo

2.6 TinkerCAD

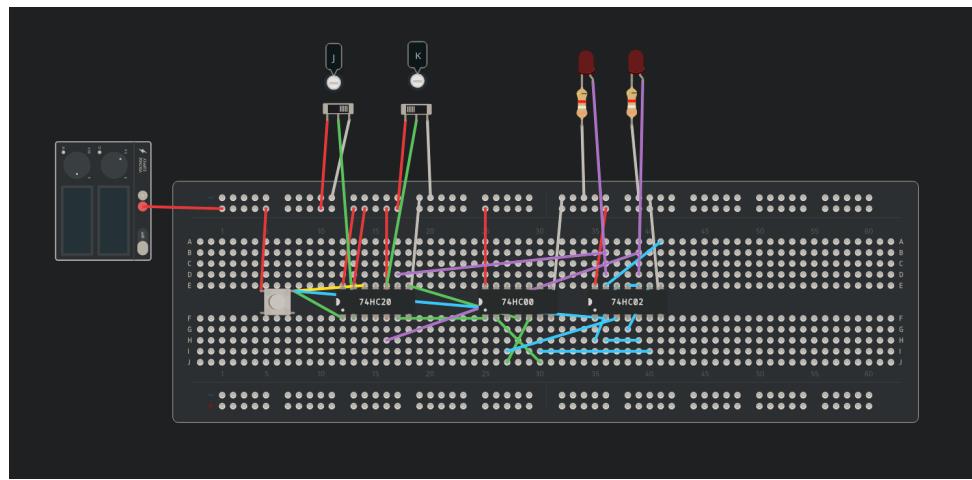


Figure 6: TinkerCAD Simulation

Here

2.7 Conclusion

We have successfully Designed and Demonstrated the working of a Master-Slave Flip-Flop

3 4-Bit Up-Down Counter

3.1 Objective

Using Arduino To implement a 4 bit ripple counter

3.2 Equipment Required

1. Digital Test Kit
2. Arduino UNO
3. Arduino IDE
4. Connecting Wire

3.3 Procedure

3.3.1 Setup

1. Connect the Arduino to the Laptop
2. Connect the outlets of the Arduino to LEDs

3.3.2 Code

Listing 1: Arduino Code

```
1 const int ledPins[4] = {2, 3, 4, 5};
2 int count = 0;
3 bool up = true;
4 unsigned long lastToggle = 0;
5 const unsigned long period = 500;
6
7 void setup() {
8     for(int i = 0; i < 4; i++){
9         pinMode(ledPins[i], OUTPUT);
10        digitalWrite(ledPins[i], LOW);
11    }
12 }
13
14 void loop() {
15     unsigned long currentTime = millis();
16
17     if(currentTime - lastToggle >= period){
18         lastToggle = currentTime;
19
20         for(int i = 0; i < 4; i++){
21             digitalWrite(ledPins[i], (count >> i) & 0x01);
22         }
23
24         if(up){
25             count++;
26         } else {
27             count--;
28         }
29     }
30 }
```

```
31     if(count >= 16){  
32         up = false;  
33         count = 15;  
34     }  
35  
36     if(count < 0){  
37         up = true;  
38         count = 0;  
39     }  
40 }  
41 }
```

3.4 Schematic

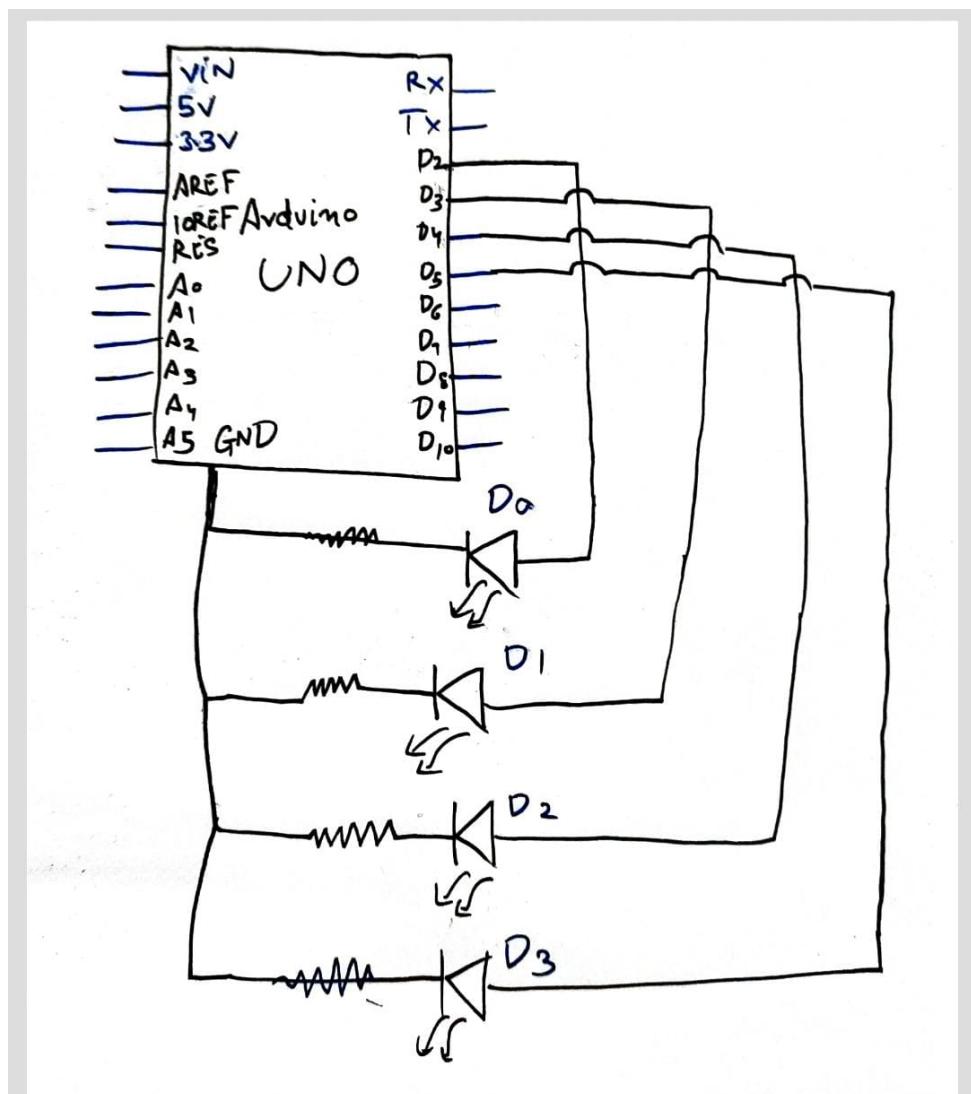


Figure 7: Schematic

3.5 Lab Photo

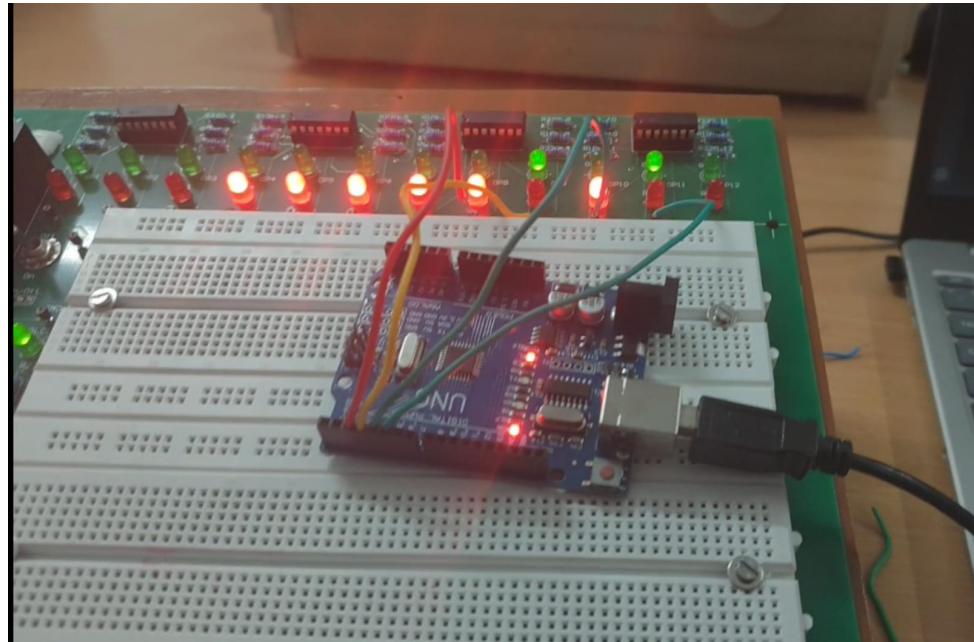


Figure 8: Lab Photo

3.6 TinkerCAD

Here

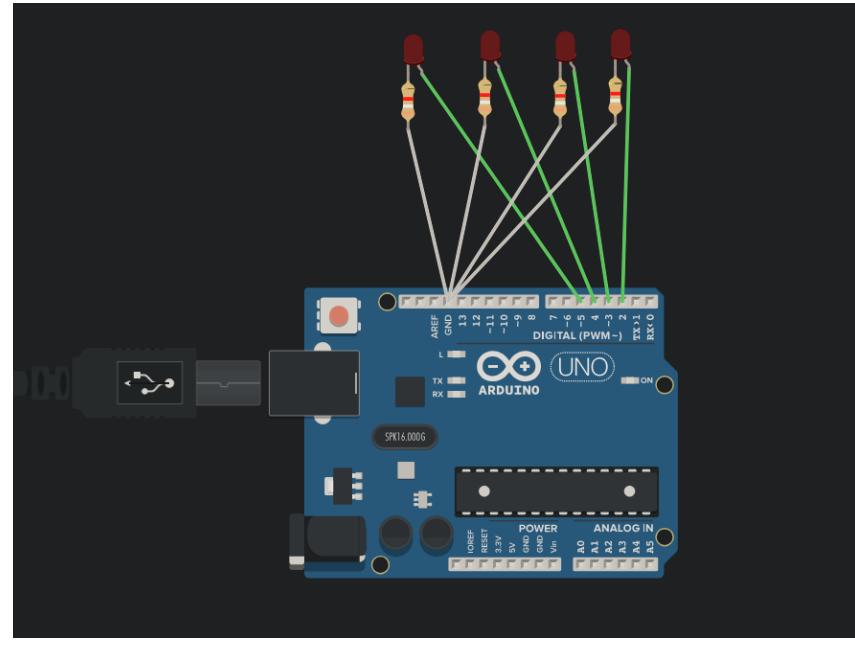


Figure 9: Arduino TinkerCAD

3.7 Conclusion

We have successfully designed and tested a 4 Bit Ripple Counter